

Mark schemes

Q1.

(a) 400 000

allow 1 mark for correct substitution ie

$$\frac{25000}{?} = \frac{800}{12800}$$

or

$$\frac{25}{?} = \frac{800}{12800}$$

2

[2]

Q2.

(a) 10 500

allow 1 mark for $75 \times 32\,200 \div 230$

2

[2]

Q3.

60

allow 1 mark for correct transformation

2

[2]

Q4.

(a) (i)
$$\frac{\text{voltage across primary}}{\text{voltage across secondary}} = \frac{\text{no of turns in primary}}{\text{no of turns in secondary}}$$

accept
$$\frac{V_P}{V_S} = \frac{N_P}{N_S}$$

or
$$\frac{V_{in}}{V_{out}} = \frac{N_{in}}{N_{out}}$$

1

(ii) $N_p = 4000$

$$\frac{25(000)}{275(000)} = \frac{N_P}{44000} \text{ for 1 mark}$$

2

(b) (i) resistance of cable decreases

1

(ii) convection (to the air)
or
conduction (to the air)
not radiation

1

[11]

Q5.

(i) iron

for 1 mark

1

(ii) 20

gains 2 marks

else working

gains 1 mark

2

(iii) reverse input/output
for 1 mark

or increase secondary turns

1

[4]

Q6.

- (a) (i) Iron
for 1 mark

1

(ii) $V/240 = 2000/10\ 000$
 $V = 48$
 V

for 1 mark each

3

[4]

Q7.

(a)

$$\frac{1.5}{5.0} = \frac{150}{N_s}$$

$$N_s = \frac{150}{0.3}$$

$$N_s = 500$$

1

1

1

[3]

Q8.

- (a) **A** primary coil
and
B secondary coil

C iron core

1

1

(b) $\frac{230}{V_s} = \frac{200}{1200}$

1

$$V_s = \frac{1200 \times 230}{200}$$

1

$$V_s = 1380 \text{ (V)}$$

1

[5]

Q9.

- (a) 80 (turns)

or credit (1) for any equation which if correctly evaluated would give 80 example

example

$$\frac{230}{5.75} = \frac{3200}{\text{number of turns}}$$

2

[7]

Q10.

- (a) (i) step-down (transformer) because fewer turns on the output/secondary (coil)

no credit for just 'step-down transformer'

accept '...less turns...'

do **not** credit '...fewer coils...'

or 'the p.d. across the input / primary will be greater than the p.d. across the output / secondary'

1

- (b) 2250

correct substitution

$$\text{eg } \frac{150}{\text{p.d. across secondary}} = \frac{500}{7500} \text{ gains 1 mark}$$

or appropriate transformation

$$\text{eg (p.d. across secondary =) } \frac{\text{number of turns on secondary}}{\text{number of turns on primary}} \times \text{p.d. across primary gains 1 mark}$$

2

[3]

Q11.

(a) step-down

1

(b) (i) 1.6

correct order only

1

12.8

1

[3]

Q12.

(a) 18

allow 1 mark for correct substitution, ie

$$\frac{230}{7.2} = \frac{575}{n_s}$$

2

[2]

Q13.

(a) (i) Iron

1

(ii) 50

*ignore references to current
reason only scores if 50 chosen*

1


*there are more turns on the secondary coil (than the primary coil)
accept it is a step-up transformer
not more coils*

1

[3]

Q14.

(a) (i)

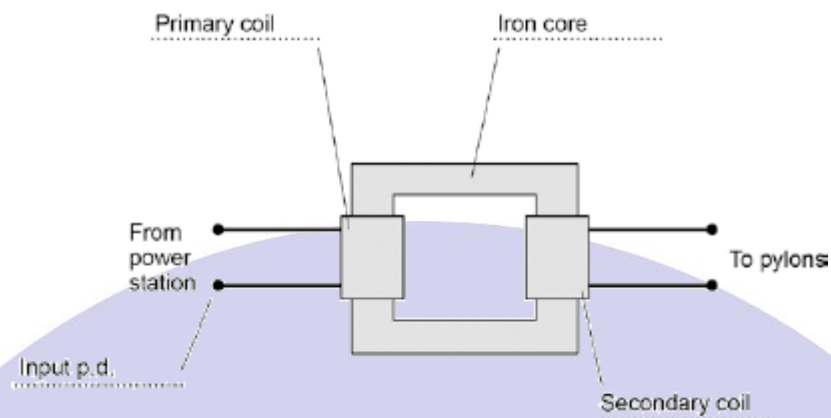

(ii) 16 000

*allow 1 mark for correct substitution
ie $400 \div 25 = n \div 1000$*

Q15.

(a) a magnetic field

*accept electromagnetic field
heat is insufficient*

that is alternating / changing

(b) 20

*allow 1 mark for correct
substitution, ie*

$$\frac{230}{11.5}$$

provided no subsequent step

Q16.

$$\frac{230}{V_s} = \frac{690}{57}$$

1

$$V_s = \frac{230 \times 57}{690}$$

1

$$V_s = 19 \text{ (V)}$$

an answer of 19 (V) scores 3 marks

1

[3]

Q17.

(a) It is easily magnetised.

1

(b) p.d. across the secondary coil is smaller (than p.d. across the primary coil)

1

(c) ratio $\frac{V_p}{V_s} = \frac{6}{12}$

$$\frac{6}{12} = \frac{50}{N_p}$$

accept any other correct ratio taken from the graph

1

$$\frac{6}{12} = \frac{50}{N_p}$$

$$N_p = 100$$

use of the correct turns ratio and substitution or correct transformation and substitution

1

$$N_p = 100$$

allow 100 with no working shown for 3 marks

1

[5]

Q18.

(a) 10

$$\frac{230}{V_s} = \frac{4600}{200}$$

allow 1 mark for correct substitution ie

2

[2]

Q19.

5.75 or 5.8 or 6(.0)

allow for **1** mark **either**

$$\frac{230}{p.d.} = \frac{20\,000}{500}$$

or

$$p.d. = 230 \div 40$$

2

V / volt(s)

1

[5]

Q20.

3067 (V)

allow all **3** marks for 3060 to 3070 (V)

$$V = \frac{230 \times 4000}{300} \quad \text{gains 2 marks}$$

$$\frac{230}{V} = \frac{300}{4000} \quad \text{gains 1 mark}$$

3

[3]

Q21.

(a)

400 000

allow **1** mark for correct substitution ie

$$\frac{25000}{?} = \frac{800}{12800}$$

or

$$\frac{25}{?} = \frac{800}{12800}$$

2

volt(s) / V

an answer 400 gains **2** marks

an answer 400 kilovolts / kV gains **3** marks

although the unit mark is independent to gain **3** marks it must be consistent with the numerical value

1

[3]

Q22.

- (a) (i) step-up

both parts required

more turns on the secondary / output (coil)

*do **not** accept coils for turns**'secondary output is greater than primary input' is insufficient*

1

- (ii) (easily) magnetised (and demagnetised)

*accept (it's) magnetic**it's a conductor negates answer*

1

- (b) 60

$$\frac{230}{15} = \frac{720}{N_s}$$

allow 1 mark for correct substitution, ie

2

[4]**Q23.**

$$\frac{230}{V_s} = \frac{2000}{40}$$

1

$$V_s = \frac{40}{2000} \times 230$$

subsequent marks can only be awarded if the first equation is correct and has been used

1

$$V_s = 4.6 \text{ (V)}$$

1

$$V_s = 4.6 \times I_s = 6.9$$

this mark may be awarded if the pd is incorrectly calculated

1

$$I_s = 1.5 \text{ A}$$

allow a correctly calculated I_s using an incorrectly calculated pd

1

OR

$$6.9 = I_p \times 230 \text{ (1)}$$

$$I_p = \frac{6.9}{230} \quad (1)$$

subsequent marks can only be awarded if the first equation is correct and has been used

$$I_p = 0.03 \text{ (A) (1)}$$

$$I_s = 0.03 \times \frac{2000}{40} \quad (1)$$

this mark may be awarded if I_p is incorrectly calculated

$$I_s = 1.5 \text{ (A) (1)}$$

allow a correctly calculated I_s using an incorrectly calculated I_p

1

[5]