


What is electricity?

What I already know:


- Electricity is a form of energy that can be carried by wires and is used for heating and lighting, and to provide power for devices.
- Sources of light and sound may need electricity to work.

New knowledge:

- Identify a range of common appliances that run on electricity.
- Construct a simple series electrical circuit, identifying and naming its basic parts, including cells, wires, bulbs, switches and buzzers.
- Investigate electrical circuits and identify whether a lamp will light in these circuits, based on whether the electrical loop is complete.
- Recognise that a switch opens and closes a circuit and associate this with whether or not a lamp lights in a simple series circuit.
- Recognise some common conductors and insulators, and associate metals with being good conductors.

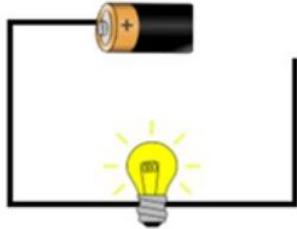

Incomplete circuit
Bulb will not light

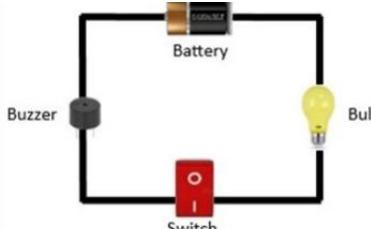

Complete circuit
Bulb will light and buzzer will sound




Observing and measuring



Asking questions



Making predictions

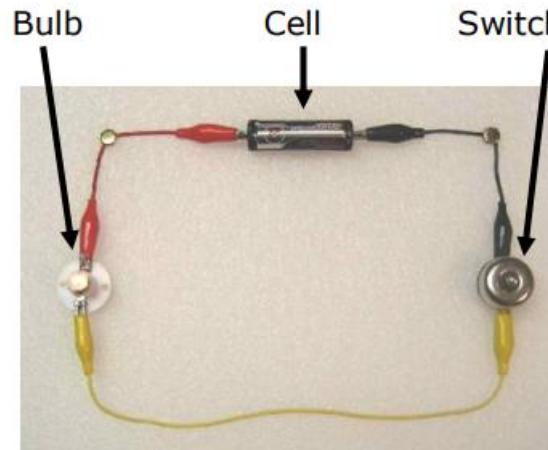

Enquiry questions:

- What common appliances use electricity?
- What components create a simple electrical circuit?
- How do switches work?
- Which materials make good conductors and insulators?
- Which famous scientists developed our understanding and use of electricity?

Scientific skills:

- Name the basic parts of an electrical circuit including cells, batteries, wires, bulbs, switches and buzzers.
- Create and test a variety of electrical circuits, including the use of switches.
- Test different materials to identify electrical conductors and insulators.

Vocabulary:

Electricity	A form of energy used for lighting, heating, making sound and making machines work.
Appliance	A device or piece of equipment designed to perform a specific function.
Circuit	A complete loop that electricity can move around.
Simple series	A circuit connected in one loop so electricity can only flow one way.
Cell	A unit that stores chemical energy and converts it into electrical energy.
Battery	A device, made of more than one cell, that can make electricity when chemicals react together.
Wire	A long, thin, flexible piece of metal that carries electricity.
Bulb	A component that uses electricity to create light.
Switch	A means of controlling the flow of electricity in the circuit.
Conductor	A material that allows electricity to pass through it easily, e.g. copper, iron and steel.
Insulator	A material that does not allow electricity to pass through it, e.g. plastic, wood and rubber.



Setting up tests



Recording data



Interpreting and communicating results



Evaluating