

## Mark Scheme

**Q1.**

A

[1]

**Q2.**

A

[1]

**Q3.**

- (a) (i) for X: ( $P = VI$  gives)  $24 = 12I$  and  $I = 2 \text{ A}$  (1)  
for Y  $18 = 6I$  and  $I = 3 \text{ A}$  (1)

2

- (b) (i)  $12 \text{ V}$  (1)

- (ii) voltage across  $R_2$  ( $= 12 - 6$ ) =  $6 \text{ (V)}$  (1)  
 $I = 3 \text{ (A)}$  (1)  
( $V = IR$  gives)  $6 = 3R_2$  and  $R_2 = 2\Omega$  (1)  
(allow C.E. for  $I$  and  $V$  from (a) and (b)(i))

$$[\text{or } V = I(R_1 + R_2) \text{ (1) } 12 = 3(2 + R_2) \text{ (1) } R_2 = 2\Omega \text{ (1)}]$$

- (iii) current =  $2 \text{ (A)} + 3 \text{ (A)} = 5 \text{ A}$  (1)  
(allow C.E. for values of the currents)

- (iv)  $27 \text{ (V)} - 12 \text{ (V)} = 15 \text{ V}$  across  $R_1$  (1)

- (v) for  $R_1$ ,  $15 = 5 R_1$  and  $R_1 = 3\Omega$  (1)  
(allow C.E. for values of  $I$  and  $V$  from (iii) and (iv))

7

[9]

**Q4.**

- (a) (i)  $5 \text{ V}$  (1)

- (ii)  $R_T = 36 (\Omega)$   
(use of  $V = IR$  gives)  $15 = I \times 36$  and  $I = 0.42 \text{ A}$  (1)

3

- (b) (i) equivalent resistance of the two lamps  $\frac{1}{R} = \frac{1}{12} + \frac{1}{12} = \frac{1}{6}$  (1)

$$R_T = 6 + 12 = 18 (\Omega) \text{ and } 15 = I \times 18 \text{ (1) (to give } I = 0.83 \text{ A)}$$

- (ii) current divides equally between lamps (to give  $I = 0.42 \text{ A}$ )  
(or equivalent statement) (1)

3

- (c) same brightness (1)  
(because) same current (1)

2

[8]

**Q5.**

- (a) (i) 6.0 ( $\Omega$ ) (1) 1
- (ii) 4.5 (V) (1) 1
- (iii) (use of  $I = V/R$ )  
 $I = 4.5/6.0 = 0.75$  (A) (1)  
 current through cell A =  $0.75/2 = 0.375$  (A) (1) 2
- (iv) charge =  $0.375 \times 300 = 112.5$  (1) C (1) 2
- (b) cells C and D will go flat first or A and B last longer (1)  
 current/charge passing through cells C and D (per second) is  
 double/more than that passing through A or B (1)  
 energy given to charge passing through cells **per second** is double  
 or more than in cells C and D (1) or in terms of power 3

[9]

**Q6.**

- (b)  $R = 1.5/0.66 = 2.3(\Omega)$  (2.27) ✓ 1
- (c) (use of  $V = IR$ )  
 $I = 1.5/(22 + 1.2) = 0.065$  ✓ (A) (0.0647) ✓ 1
- (d) current in  $R_1 = 0.66 - 0.0647 = 0.595$  (A) ✓  
*CE from 4.2/4.3* 1  
 resistance of  $R_1$  and probe =  $1.5/0.595 = 2.52$  ( $\Omega$ ) ✓  
*alternative method:  $1/2.3 = 1/23.2 + 1/(R_{probe} + 2.4)$  ✓* 1  
 resistance of probe =  $2.52 - 2.4 = 0.12$  ( $\Omega$ ) ✓  
*correct rearrangement ✓*  
*range 0.1 – 0.15 ✓*  
*accept 1 sig. fig. for final answer* 1

- (f) ANY TWO FROM  
 correct reference to lost volts OR terminal pd OR reduced current ✓  
 reference to resistors not changing OR resistors constant ratio ✓  
 reference to voltmeter having high/infinite resistance (so not affecting circuit) ✓  
 reference to pd between AB being (very) small (due to  
 closeness of resistance ratios in each arm) ✓  
 voltmeter (may not be) sensitive enough ✓

1  
1

[7]

**Q7.**

A

[1]